

## Intergrated Circuits report 2

- ※ 과제는 A4용지에 자필로 작성한뒤 스테이플러로 제본하여 제출해 주시기 바랍니다.
- ※ 과제는 Intergrated Circuit Design Fourth Edition 기준으로 출제되었습니다.

1.8

Sketch a transistor-level schematic for a compound CMOS logic gate for each of the following functions:

- a)  $Y = \overline{ABC + D}$
- b)  $Y = \overline{(\overline{AB + C}) \cdot D}$
- c)  $Y = \overline{AB + C \cdot (A + B)}$

1.10

Draw a transistor-level schematic for the latch of Figure 1.75.

 


FIGURE 1.75 Level-sensitive latch stick diagram

1.21

Consider the design of a CMOS compound OR-OR-AND-INVERT (OAI22) gate computing  $F = \overline{(A + B) \cdot (C + D)}$ .

- a) sketch a transistor-level schematic
- b) sketch a stick diagram
- c) estimate the area from the stick diagram

2.4

Show that the current through two transistors in series is equal to the current through a single transistor of twice the length if the transistors are well described by the Shockley model. Specifically, show that  $I_{DS1} = I_{DS2}$  in Figure 2.32 when the transistors are in their linear region:  $V_{DS} < V_{DD} - V_t$ ,  $V_{DD} > V_t$  (this is also true in saturation). *Hint:* Express the currents of the series transistors in terms of  $V_1$  and solve for  $V_1$ .

 


FIGURE 2.32 Current in series transistors

2.7

Calculate the diffusion parasitic  $C_{db}$  of the drain of a unit-sized contacted nMOS transistor in a  $0.6\ \mu\text{m}$  process when the drain is at 0 and at  $V_{DD} = 5\ \text{V}$ . Assume the substrate is grounded. The transistor characteristics are  $CJ = 0.42\ \text{fF}/\mu\text{m}^2$ ,  $MJ = 0.44$ ,  $CJSW = 0.33\ \text{fF}/\mu\text{m}$ ,  $MJSW = 0.12$ , and  $\psi_0 = 0.98\ \text{V}$  at room temperature.

2.17

A novel inverter has the transfer characteristics shown in Figure 2.34. What are the values of  $V_{IL}$ ,  $V_{IH}$ ,  $V_{OL}$ , and  $V_{OH}$  that give best noise margins? What are these high and low noise margins?

 


FIGURE 2.34  
Transfer characteristics

2.21

Suppose  $V_{DD} = 1.2\ \text{V}$  and  $V_t = 0.4\ \text{V}$ . Determine  $V_{out}$  in Figure 2.36 for the following. Neglect the body effect.

- $V_{in} = 0\ \text{V}$
- $V_{in} = 0.6\ \text{V}$
- $V_{in} = 0.9\ \text{V}$
- $V_{in} = 1.2\ \text{V}$

 


FIGURE 2.36  
Single pass transistor

3.3

Sketch a 2-input NOR gate with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter. Compute the rising and falling propagation delays of the NOR gate driving  $b$  identical NOR gates using the Elmore delay model. Assume that every source or drain has fully contacted diffusion when making your estimate of capacitance.

3.10

An output pad contains a chain of successively larger inverters to drive the (relatively) enormous off-chip capacitance. If the first inverter in the chain has an input capacitance of  $20\ \text{fF}$  and the off-chip load is  $10\ \text{pF}$ , how many inverters should be used to drive the load with least delay? Estimate this delay, expressed in FO4 inverter delays.

3.17

Consider a process in which pMOS transistors have three times the effective resistance as nMOS transistors. A unit inverter with equal rising and falling delays in this process is shown in Figure 4.42. Calculate the logical efforts of a 2-input NAND gate and a 2-input NOR gate if they are designed with equal rising and falling delays.

 


FIGURE 4.42  
Unit inverter