

Digital Engineering 2nd report

● 제출 : 4월 22일(화) 수업시간

● 디지털 공학 과제 주의사항


1. 과제는 반드시 **자필**로 작성하셔야 합니다.
2. **문제 풀이 과정**이 다 들어가 있어야 하면, 답에는 반드시 **밑줄이나 박스** 등의 답을 알아볼 수 있는 표기 바랍니다.
3. **A4용지**에 반드시 **학번 이름**을 포함하여 제출 바랍니다.
4. 문제는 **7판 원서** 기준으로 출제되었습니다.
5. 스테이플러는 종이 **왼쪽**에 찍어주시기 바랍니다.
6. 문제의 순서가 명확하도록 **페이지 번호** 표기바랍니다.
7. 풀이과정을 알아볼 수 없는 경우 불이익이 발생할 수 있습니다.

4.8 A switching circuit has four inputs as shown. A and B represent the first and second bits of a binary number N_1 . C and D represent the first and second bits of a binary number N_2 . The output is to be 1 only if the product $N_1 \times N_2$ is less than or equal to 2.

(a) Find the minterm expansion for F .

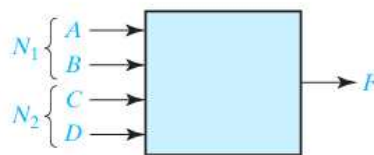(b) Find the maxterm expansion for F .

Express your answers in both decimal notation and algebraic form.



4.25 Four chairs are placed in a row:



Each chair may be occupied (1) or empty (0). Give the minterm and maxterm expansion for each logic function described.

(a) $F(A, B, C, D)$ is 1 iff there are no adjacent empty chairs.

(b) $G(A, B, C, D)$ is 1 iff the chairs on the ends are both empty.

(c) $H(A, B, C, D)$ is 1 iff at least three chairs are full.

(d) $J(A, B, C, D)$ is 1 iff there are more people sitting in the left two chairs than in the right two chairs.

4.27 Given $f(a, b, c) = a(b + c')$.

- (a) Express f as a minterm expansion (use m -notation).
- (b) Express f as maxterm expansion (use M -notation).
- (c) Express f' as a minterm expansion (use m -notation).
- (d) Express f' as a maxterm expansion (use M -notation).

5.3 Find the minimum sum of products for each function using a Karnaugh map.

- (a) $f_1(a, b, c) = m_0 + m_2 + m_5 + m_6$
- (b) $f_2(d, e, f) = \Sigma m(0, 1, 2, 4)$
- (c) $f_3(r, s, t) = rt' + r's' + r's$
- (d) $f_4(x, y, z) = M_0 \cdot M_5$

5.14 Find the minimum sum-of-products expressions for each of these functions.

- (a) $f_1(A, B, C) = m_1 + m_2 + m_5 + m_7$
- (b) $f_2(d, e, f) = \Sigma m(1, 5, 6, 7)$
- (c) $f_3(r, s, t) = rs' + r's' + st'$
- (d) $f_4(a, b, c) = m_0 + m_2 + m_3 + m_7$
- (e) $f_5(n, p, q) = \Sigma m(1, 3, 4, 5)$
- (f) $f_6(x, y, z) = M_1M_7$

5.37 The function $F(A, B, C, D, E) = \Sigma m(1, 7, 8, 13, 16, 19) + \Sigma d(0, 3, 5, 6, 9, 10, 12, 15, 17, 18, 20, 23, 24, 27, 29, 30)$.

- (a) Draw a Karnaugh map for f .
- (b) Find all prime implicants of f . (Prime implicants containing only don't-cares need not be included.)
- (c) Find all minimum sum of products for f .
- (d) Find all prime implicants of f' .
- (e) Find all minimum product of sums for f .